

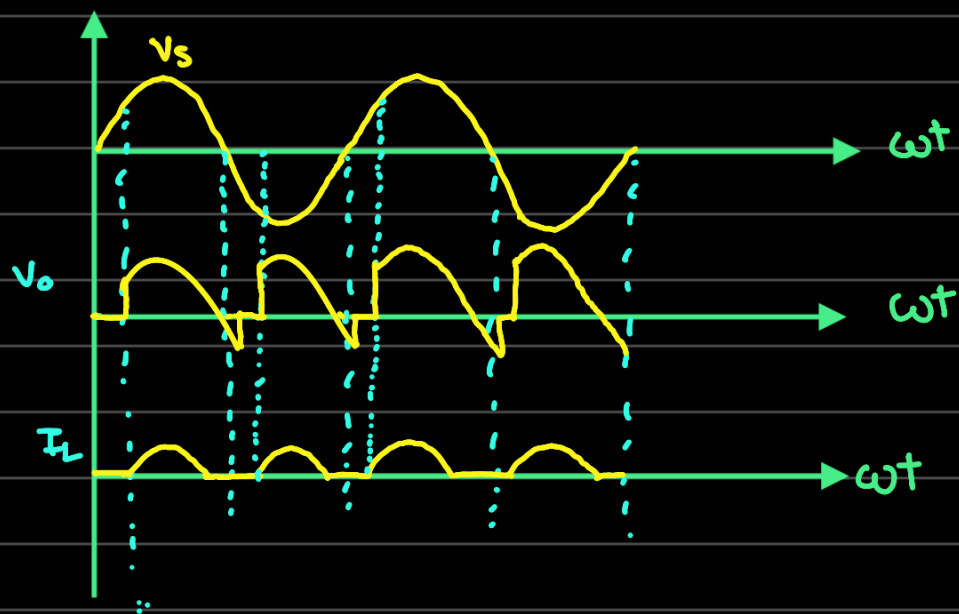


Day-8

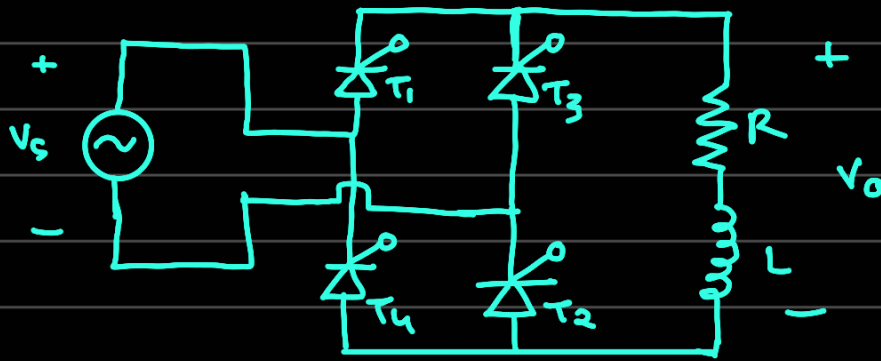

Assumed I_L is discontinuous

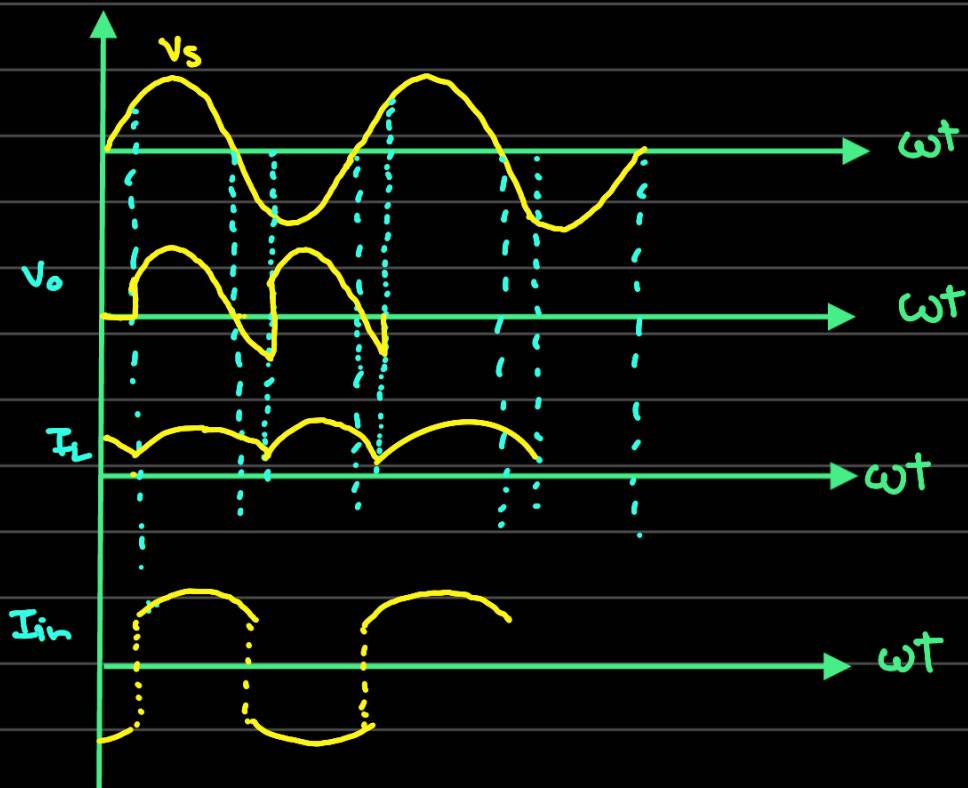

$$V_s = V_m \sin \omega t$$

If continuous conduction,


$$V_o = -V_m \sin \omega t, \quad 0 < \omega t < \omega t_1$$

$$= V_m \sin \omega t, \quad \omega t_1 < \omega t < \pi + \omega t_1$$

$$= -V_m \sin \omega t, \quad \pi + \omega t_1 < \omega t < 2\pi + \omega t_1$$

$$V_{o \text{ avg}} = \frac{1}{T} \int_0^T V_o dt$$

$$= \frac{2V_m}{\pi} \cos \alpha$$

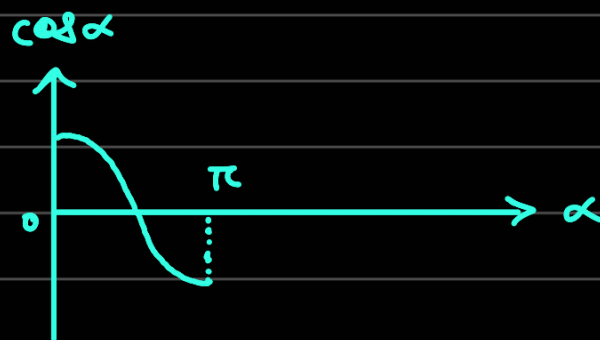

$V_{o \text{ avg}}$ can be -ve. Not possible with diodes. Power can be pushed back to source.

(Inverter!)