

EN313 Power Electronics

Basic OpAmp Configurations & Loading Effects

S. Ravi Prakash Reddy

Assistant Professor
Department of Energy Science & Engineering
Indian Institute of Technology Bombay

Potential divider

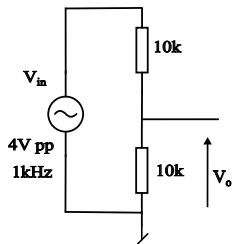


Figure 1: Potential divider

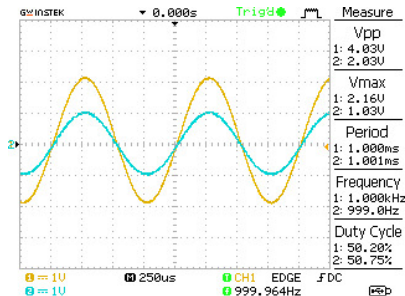


Figure 2: V_{in} and V_o

- Output voltage

$$V_o = \frac{10k}{10k + 10k} * V_{in} = 2V \text{ (pk-pk)} \quad (1)$$

Potential divider: Loading effects

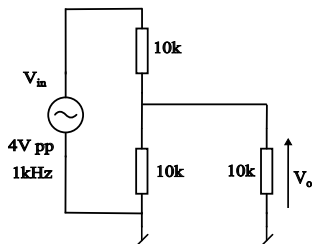


Figure 3: Potential divider: loading

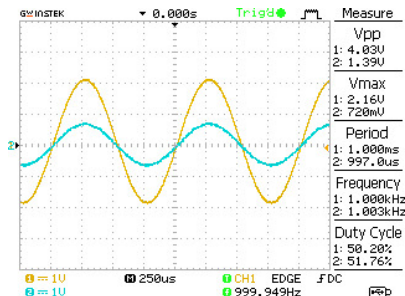


Figure 4: V_{in} and V_o

- Due to loading, output voltage (V_o) dips !!
- How to take care of this?
- One must ensure that negligible current is drawn from output of potential divider to address loading effects.

Buffer/Unity-gain Amplifier

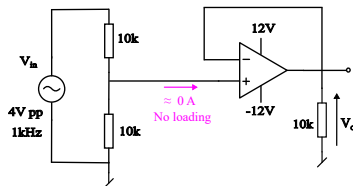


Figure 5: Opamp buffer

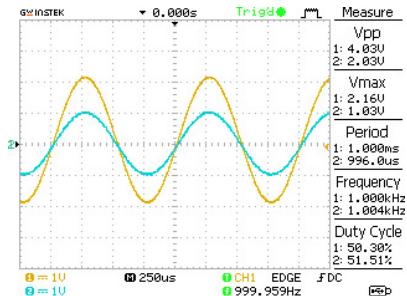


Figure 6: V_{in} and V_o

Buffer/Unity-gain Amplifier/Voltage Follower

- Opamp buffer can be used at the output stage of potential divider to get rid of loading effects.
- Input resistance of opamp buffer is very high.

$$R_{in} \approx R_i (1 + A_v)$$

- Output resistance of opamp buffer is very low.

$$R_{out} \approx \frac{R_o}{(1 + A_v)}$$

- A_v : Open-loop gain of opamp (2×10^5 V/V for LM741)
 R_i : Input resistance of opamp ($2 \text{ M}\Omega$ for LM741)
 R_o : Output resistance of opamp ($75 \text{ }\Omega$ for LM741)

Non-inverting Amplifier

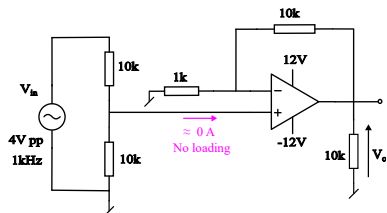


Figure 7: Non-inverting configuration

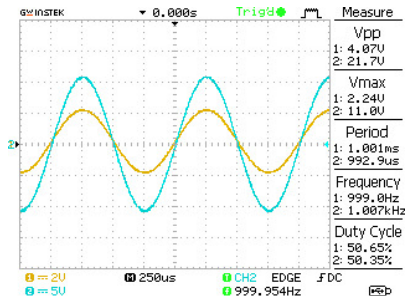


Figure 8: V_{in} and V_o

Non-inverting Amplifier

- In this configuration, opamp gets its input directly at the inverting terminal.
- Thus, it is not prone to loading effects because of very high input impedance.
- The input resistance for this configuration is given by

$$R_{in} \approx R_i A_v \frac{R_1}{R_1 + R_2}$$

Inverting Amplifier

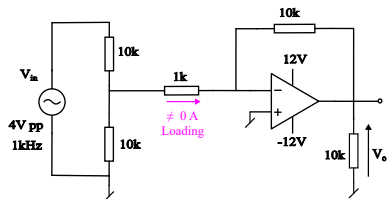


Figure 9: Inverting configuration: loading

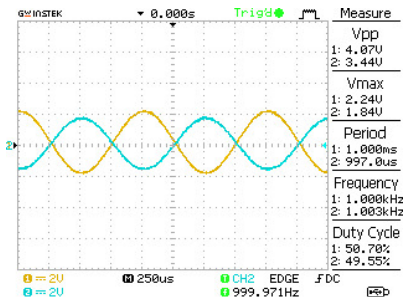


Figure 10: V_{in} and V_o

Inverting Amplifier: Loading effects

- Inverting amplifier configuration is prone to loading effects (on the input side).
- This is because the input resistance of this configuration is low as compared to that of non-inverting configuration.

$$R_{in} \approx R_i$$

Buffer + Inverting Amplifier

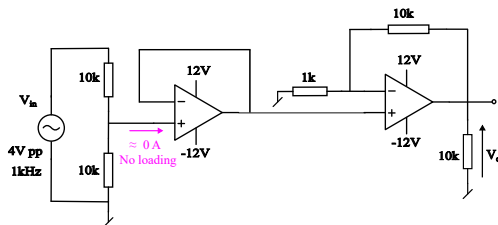


Figure 11: Buffer with inverting config.

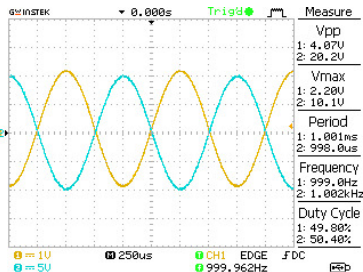


Figure 12: V_{in} and V_o

- A buffer can be placed at the front-end of inverting amplifier to get rid of loading effects.

Saturation effects in Opamp

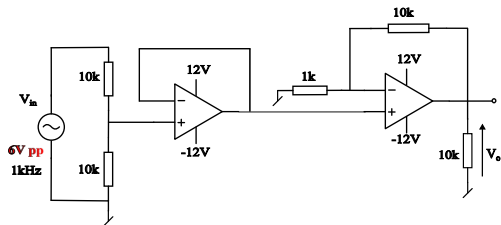


Figure 13: Buffer with inverting config.

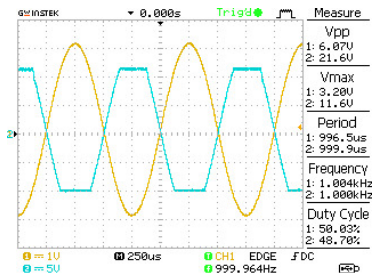


Figure 14: V_{in} and V_o

- Input is 6V (pk-pk), expected o/p voltage is $6 \times 0.5 \times 10 = 30\text{V}$ (pk-pk).
- Opamp supply is $\pm 12\text{V}$, output voltage saturates at 21.6 V pp.
- The remaining drop (24-21.6 V) is due to saturation voltages of transistors present in opamp.

Slew rate in Opamp

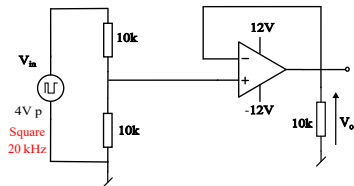


Figure 15: Buffer: slew rate effect on output with 20 kHz square input

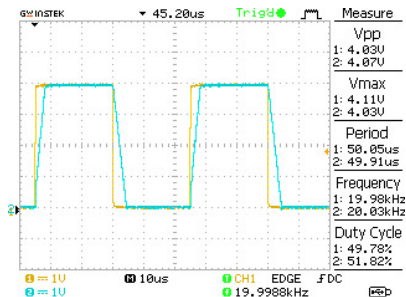


Figure 16: V_{in} and V_o

Slew rate in Opamp: 100kHz input source

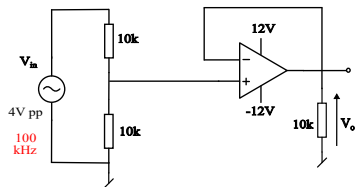


Figure 17: Buffer: slew rate effect on output with 100 kHz input

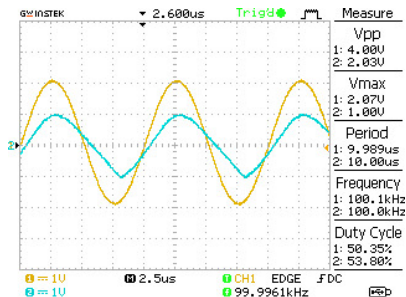


Figure 18: V_{in} and V_o

Slew rate in Opamp: 500kHz input source

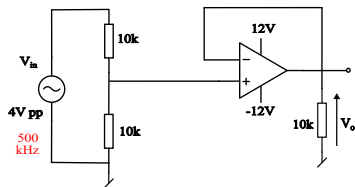


Figure 19: Buffer: slew rate effect on output with 500 kHz input

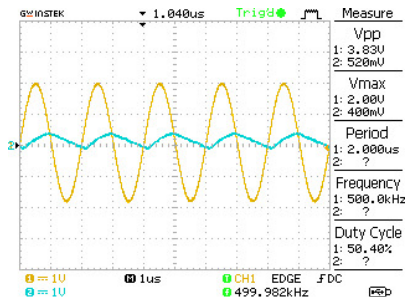


Figure 20: V_{in} and V_o

THANK YOU